



Institute of Technology of Cambodia

Department of Electrical and Energy Engineering



Course Title:

Analog Electronics

npn BJT as cabinet Drawer Electric Door Lock

Group 4:

1.SOK SEANGHAI

2.SOK SOPHORS

3.SOK THYRITH

4.SOK VATHANAK

5.SOM CHANTOLA

6.SOM SOMBATHROTANAK

Calculator

Calculator

Edit Slides

Build Circuit

Leader

Researcher


Components



Power Supply




Door lock

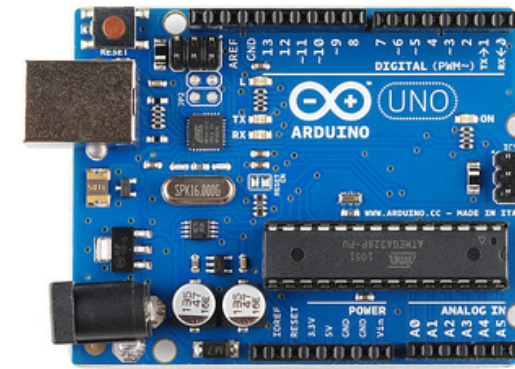

Arduino




resistor

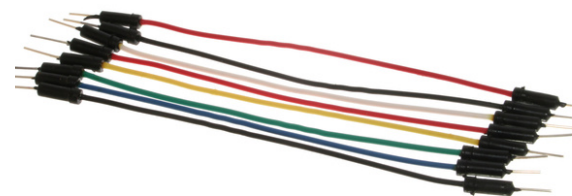

jumper wires



Transistor


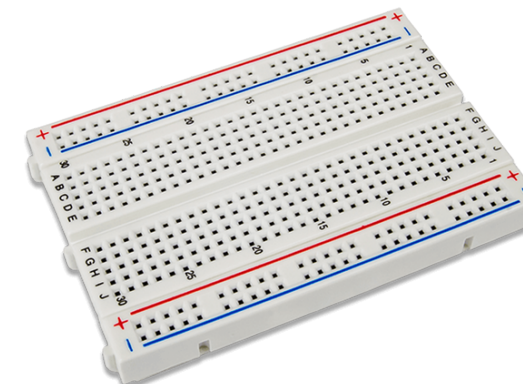


breadboard



push button

The process

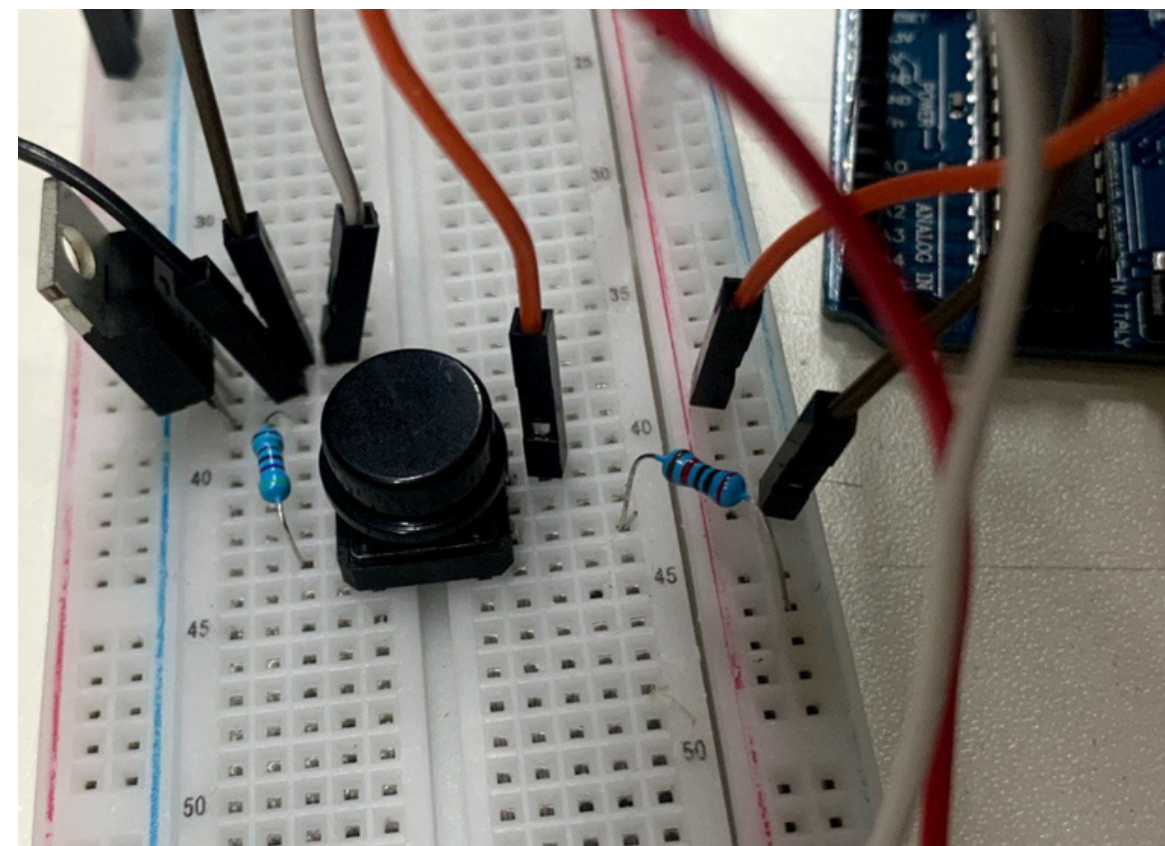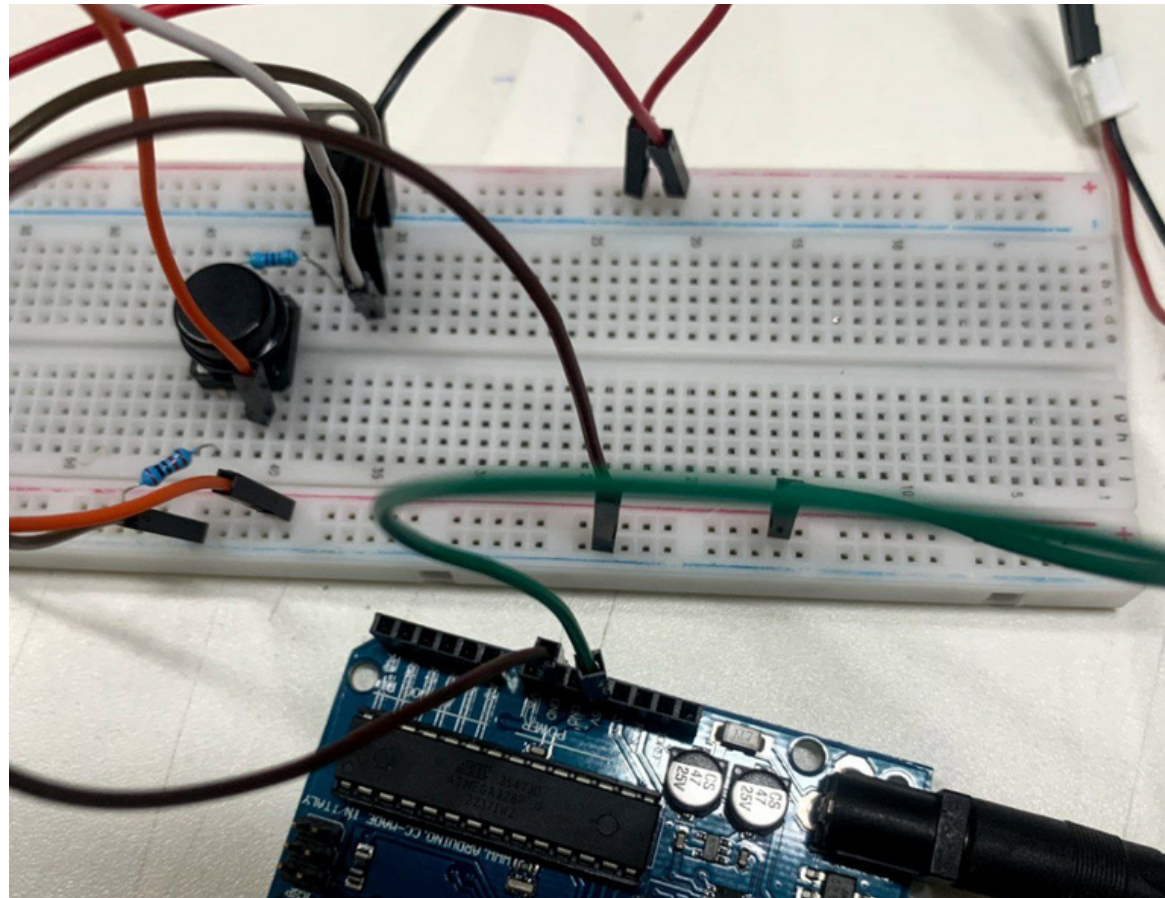

1. Connect the lock to the positive terminal of the power supply and the other to the collector of the transistor(1RF630N).



2. Connect the emitter of the transistor to the ground of the power supply and Arduino. Then Connect a 4.7kΩ resistor from the base of the transistor to the terminal of button.




3. Connect the other terminal of the push button switch to the ground of the terminal 5V of Arduino. Connect a 20kΩ resistor from button to ground of Arduino.



3. Finally we supply 12V that connected terminal of lock and collector and 5v from Arduino to button on breadboard. All of connect using jumper wires.

Result of process

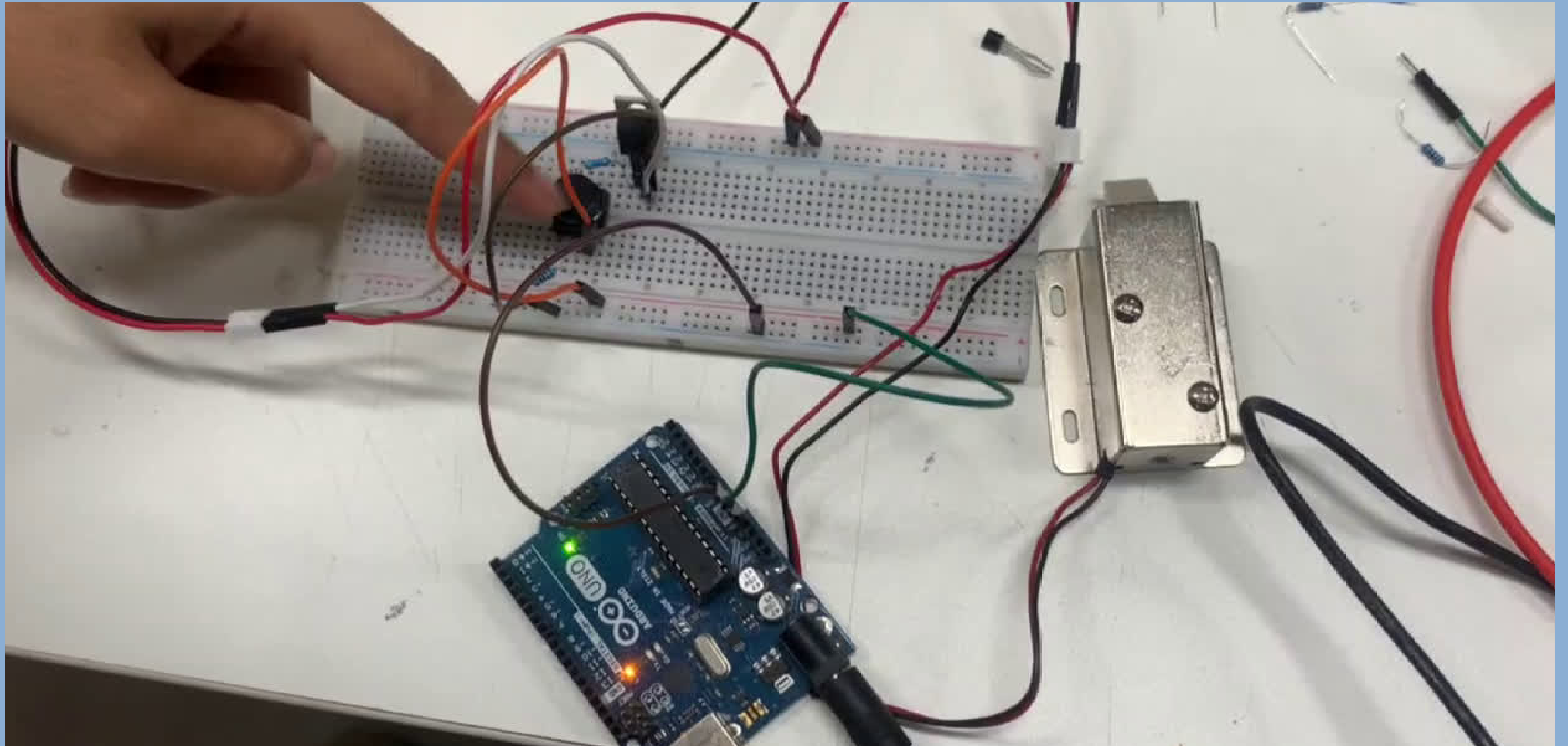

Calculation

Assume transistor is biased in Forward-active mode:

on circuit we assume $R_B = 4.7\text{k}\Omega$, $V_{(BE)on} = 0.7\text{V}$, $\beta = 150$
and we have $V_B = 5\text{V}$, $V_C = 12\text{V}$

By KVL, Then base current is:


$$I_B = (V_B - V_{(BE)on}) / R_B = 0.91\text{mA}$$

So, the collector current is:

$$I_C = \beta I_B = 136.5\text{mA}$$

The emitter current is:

$$I_E = (1 + \beta) I_B = 137.41$$

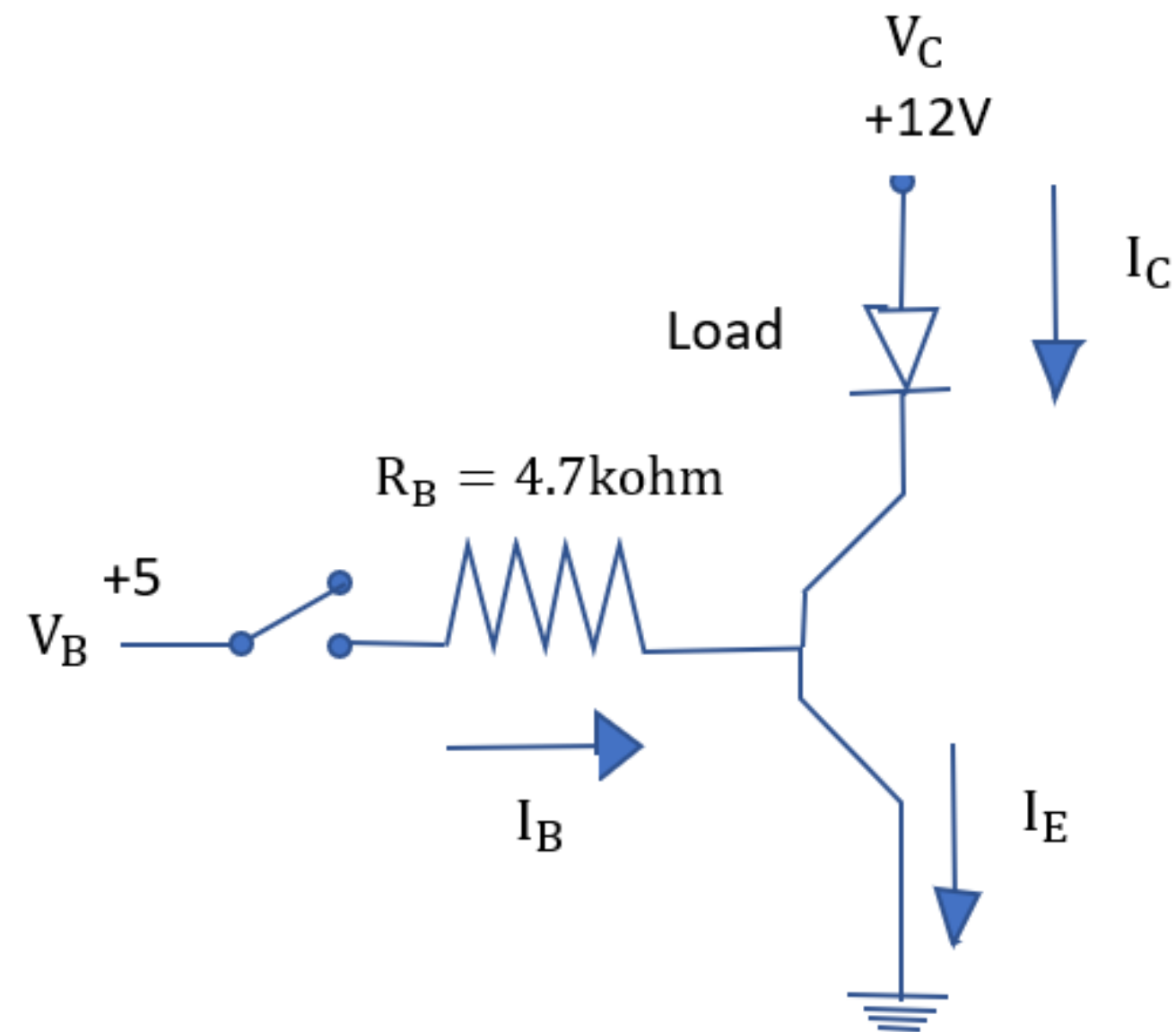



Thank you!

